CLASS G High Efficiency HI-FI Amplifier

A new high-efficiency audio amplifier circuit that can reduce the size, weight and cost of future hi-fi amplifiers. Here's an inside look at the theory and circuitry

SOME TIME AGO, THE AUDIO INDUSTRY WAS startled by the announcement that Infinity Systems, Inc. (best known for their loudspeaker systems) had come up with a more efficient way to build audio power amplifiers. They called the technique "Class D" amplification. Briefly, the system involves the use of high-frequency (in excess of 200 kHz) pulses that are first modulated by the audio signal to be amplified and then decoded by an integrating circuit that restores the audio envelope or waveshape. Since the duty cycle of each high-frequency pulse is relatively short, conduction of the output transistors is such that heat dissipation is a fraction of that encountered with more conventional Class-B circuits and overall efficiency (at least when the amplifier delivers close to its maximum power output) is high. Thus far, the product has not reached the consumer market but Infinity claims that all production problems have been licked and that the Class D, or "switching" amplifier will soon be a commercial reality.

In the meanwhile, other companies have been working on improving the efficiency of audio amplifiers. This work is so widespread, in fact, that the Hitachi Company of Japan (whose approach to better amplifier efficiency is the subject of this article) has had to change the name of their invention from Class E (which they had first proposed to use) all the way to Class G, the designation they currently plan to assign to the new and innovative circuitry we will describe here.

Class-B efficiency

When a Class-B audio amplifier delivers its maximum rated power, its efficiency (power delivered to the load divided by power used by the amplifier is quite high -70% or more. Studies show, however, that under music listening conditions, an

LEN FELDMAN* CONTRIBUTING HI-FI EDITOR

audio amplifier is called upon to deliver full or nearly full output for only a very small fraction of the time it is operating. Figure 1 represents the results of studies







FIG. 2-CLASS-B EFFICIENCY at various percentages of maximum output.

of a variety of musical selections. It shows that while music may reach peaks of +14dB (referred to a 0-dB average power level), for much of the time, actual power levels are even well below the 0-dB average level. In fact, for nearly 50% of the time (Fig. 1, left vertical scale), power levels are some 30-dB below the 0-dB point, while a + 10-dB level is reached for only 0.7% (Fig. 1, right hand vertical scale) of the time. Even allowing for highly compressed music (in which dynamic range is restricted and music is therefore more uniformly "loud") and assuming only a 10-dB crest-factor (average power is 10% of peak power), we can see from the curve of Fig. 2 (efficiency of a Class-B circuit versus the ratio of actual output to designed maximum output) that for most of the time that an amplifier of this type is reproducing music, it is operating at approximately 20% efficiency.

The Class-G idea

Hitachi's invention is designed to enable amplifiers to operate more efficiently over more of their operating range, based upon the way in which they are called upon to actually amplify musical signals. The simple diagram of Fig. 3 illustrates the Class-G idea. The input voltage, V_{in} , is the signal to be amplified and it is ap-



FIG. 3-BASIC CLASS-G amplifier.

AUGUST 1976

plied to the base of transistors Q1 and Q2. A load resistor, R_L , is connected to the emitter of Q1. Supply voltage V_1 is applied through diode D1 to the collector Q1 and the emitter of Q2. The collector of Q2 is connected to a second supply voltage V_{ce} that is higher than supply voltage V1.

Operation of the circuit is as follows: If input signal voltage V_{in} is lower than V1, Q2 is reverse biased between its base and its emitter and is therefore cut off. Current flowing through load R_L is supplied from V1 through diode D1. Under these conditions, the instantaneous efficiency of the circuit is given as: Efficiency (%) $\equiv V_{in}/$ V1. If the signal voltage increases to a value beyond that of V1 (but less than Vec), transistor Q2 becomes forward biased and is turned on. Current flowing through load R_L is now supplied from the second, higher supply-voltage Vcc through Q2. If we neglect saturation voltage between collector and emitter of Q2 (assuming it is sufficiently low), the instantaneous efficiency of the circuit is given as: Efficiency (%) $\equiv V_{in}/V_{cc}$.

Figure 4 represents the two efficiency



FIG. 4—INCREASED EFFICIENCY results from two-level power-supply system in Class-G amplifier.

levels of the system and the vertical line represents the point at which the supply voltage transition takes place. Thus, in the lower ranges of input signal voltage, the efficiency of this circuit is improved considerably and the amount of heat generated in the output transistor is reduced compared with conventional Class-B amplifiers. Referring once more to Fig. 3, it should be noted that diode D1 also serves to prevent current flowing from the higher supply-voltage source (V_{ee}) from flowing back into the first power source V1.

The thermal efficiency of the system will, of course, depend upon the choice of the two power-supply operating voltages.



FIG. 5–EFFICIENCY OF CLASS-G amplifier depends upon V_1/V_{ec} ratio.

Figure 5 compares the efficiency level at various outputs (expressed as a fraction of maximum design output) for two different Class-G designs having different V1/V_{cc} ratios as compared with conventional Class-B operation. Regardless of whether V1 is half or two thirds as great as V_{cc}, we see that efficiency is far greater than that of Class-B operation, particularly at lower output levels where, as we have seen earlier, the amplifier is likely to operate most of the time when reproducing actual music programs.

Along with improvement in efficiency comes reduced internal heat dissipation of the output devices used in the Class-G approach. Figure 6 illustrates this point for



various $V1/V_{ec}$ ratios. Internal dissipation is plotted as a fraction of maximum power output on the vertical axis, while the ratio of output power to designed maximum power is shown along the horizontal axis of the graph. As expected, internal dissipation is lower at all operating conditions for Class-G compared with conventional Class-B operation.

Distortion

Closer examination of Fig. 3 points up certain problems that exist in the basic concept of Class G. In the simple form



FIG. 7-DISTORTION that would result from simplest form of Class-G circuit.



FIG. 8-SWITCHOVER DISTORTION is reduced by the addition of diode D2.

of the circuit shown, Q2 is not turned on until input signal voltage exceeds the collector voltage of Q1 by an amount equal to the base-emitter voltage $V_{\rm be}$ of Q2. Thus, when the value of input signal voltage $V_{\rm in}$ is in the range between V1 and V1 + $V_{\rm be}$, Q1 is already saturated (between collector and emitter) before conduction of Q2 begins. This results in a distorted output waveform signal as shown in Fig. 7.

To prevent this form of distortion during the changeover from one power supply level to the other, the circuit must be modified so that saturation of Q1 does not occur until Q2 is turned on. This is accomplished by adding another diode, D2, as shown in the simplified schematic of Fig. 8. Now, when V1 is less than the input signal, the voltage between the collector and the emitter of Q1 is lower than the saturation level by an amount equal to the threshold value of D2 and thus Q1 remains unsaturated. Diode D2 may be a Zener diode or even a resistor since it is only required to maintain a voltage difference equal to the Vbe voltage of Q2. Still another diode, D3, is added to the basic circuit as shown in Fig. 7. Since a reverse bias is applied between the base and emitter of Q2 when the signal voltage is lower than supply voltage V1, the baseemitter junction of Q2 must be able to stand a reverse voltage higher than V1. Since the maximum inverse voltage of the base-emitter circuit of most transistors is generally low, diode D3 is provided to prevent the flow of reverse current through the base-emitter junction of Q2, thus protecting this junction against the reverse voltage.

Push-Pull operation

Figure 9 shows the required configura-



FIG. 9-PUSH-PULL Class-G amplifier.



FIG. 10-VOLTAGE AND CURRENT relationships in push-pull Class-G amplifier.

not turned on ceeds the colamount equal v_{be} of Q2. ut signal voltween V1 and aturated (be-) before cons results in a n signal as

istortion dure power suprcuit must be f Q1 does not n. This is acer diode, D2. schematic of ess than the ween the co! is lower than ount equal to and thus Qi D2 may be istor since it in a voltage oltage of Q2 added to the g. 7. Since : een the base ignal voltage V_1 , the baset be able to er than V1. oltage of the transistors is provided to erse current ction of Q2, against the

ed configura-





ENT relation-

tion for a push-pull output circuit. Diodes D2 and D3 shown in Fig. 8 have been omitted for the sake of clarity. Two values of positive and negative supply voltages are required and transistors Q3 and O4 operate at opposite polarity voltages compared with Q1 and Q2 to form the familiar complementary configuration (NPN nd PNP pairs are used). Fig. 10-a shows the input signal waveform, together with the voltage levels V_{c1} and V_{c2} (for the first half of the cycle) and Vcs and Vc4 for the opposite half of the signal waveform. Fig. 10-b shows the current waveforms resulting from the four supply-voltages (two voltages for each polarity). Fig. 10-c represents that portion of the output waveform powered by the lower-level supply voltage Vc1, while Fig. 10-d shows the contribution of output waveform powered by the higher supply voltage Vc2. Finally, Fig. 10-e shows a comparison of power losses (or dissipation) in Q1 and Q2 (for the half cycle shown) as compared with the power loss that would take place in a conventional Class-B configuration.

Practical Class-G circuit

The first product which Hitachi intends to introduce that will incorporate the Class-G principle is their Model SR-903 AM/FM stereo receiver, pictured in Fig. 11. By way of illustrating the improvement



FIG. 11-HITACHI SR-903 stereo receiver uses Class-G output circuit.



FIG. 12—HITACHI HMA-8300 power amplifier will be introduced in the near future and will contain Class-G output circuitry.

in efficiency attained because of this new output circuit, Dr. Gentaro Miyazaki of Hitachi Consumer Products Research Center was kind enough to supply me with some advance comparisons between this 75 watts-per-channel receiver (from 20-Hz to 20-kHz, 8-ohm loads, 0.3% maximum THD) and a typical Class-B unit having the same FTC power rating. The SR-903 will weigh in at 28.7 lbs as against 40.8 lbs for the Class-B unit. Under "music power" measurement conditions (abandoned by the industry since the advent of the FTC power rule, but nevertheless indicative of the short-term power output capability of an amplifier), the SR-903 will deliver 160 watts-per-channel



FIG. 13-OUTPUT CIRCUIT of the Hitachi HMA-8300 power amplifier.



FIG. 14-DISTORTION resulting from storage time delay in Class-G circuit.



FIG. 15-DISTORTION resulting from storage time delay is reduced by the addition of L1 to circuit.

as opposed to 110 watts-per-channel for the Class-B unit against which it was compared.

Hitachi plans to introduce many more units employing Class-G circuitry. Typical of these will be the stereo power amplifier, model HMA-8300, pictured in Fig. 12. A circuit of the power output stages of this unit is shown in the schematic diagram of Fig. 13. In addition to the circuit elements already described, we see one more refinement that should be mentioned. Note, that in series with supply voltages V_{C1} and V_{C3} are small inductors L1 and L3. Because transistors have finite turn-on and turn-off times, a form of distortion can be introduced to the output waveform as illustrated in the waveforms of Fig. 14. This form of dstortion is due to an effect known as storage time-delay and is quite independent of the base-emitter Vbe voltage discussed earlier. To counteract this effect (and to further reduce output waveform distortion in Class-G circuits), a coil is added in series with diode D6 shown in the improved circuit of Fig. 15.

The effect of storage delay would be



FIG. 16—THD VS. POWER OUTPUT at 20-kHz before and after addition of L1 (Fig. 15) in circuit. Distortion characteristic at 1-kHz is also shown.

particularly noticeable when reproducing high frequencies, since the time required for amplification of a single cycle of a 20 kHz signal is only 50 microseconds. The curves of distortion versus output measured at 1 kHz and 20 kHz for a typical Class-G circuit shows clearly that without (continued on page 87)

CLASS-G AMPLIFIERS

(continued from page 49)

the addition of the extra coils (L1 and L3) in the circuit of Fig. 13, harmonic distortion would rise more rapidly for a 20 kHz signal while remaining at a much lower level for lower frequency signals. With the addition of this final refinement, total harmonic distortion is maintained at very low levels for both md- and high-frequencies, as shown by the solid-line 20-kHz curve of Fig. 16.

FTC and Class-G

The Class-G circuit seems to be particularly attractive at this time in light of the pre-conditioning tests now required by the FTC in connection with determining the power output ratings of audio amplifiers. As many readers know, the FTC requires that amplifiers be able to sustain one third of their rated continuous power output for one hour. In Class-B circuits, this power level results in almost the greatest internal heat dissipation for the output devices and, in many cases, this has forced designers to increase heat-sink dimensions (and cost to consumers) without really providing audible benefit to users. On the other hand, Class-G operation can result in very nearly the most efficient operation at this one-third rated point (and at lower levels more often encountered in musical reproduction) with appropriate economies in weight, powersupply demands and, most important of all, retail prices that the consumer has to pay for high-quality audio amplification. R-E

*The author is indebted to Dr. Gentaro Miyazaki of Hitachi for allowing us to publish the first definitive description of Hitachi's innovative new amplifier circuit. Several claims of a pending U.S. (as well as foreign) patent have already been allowed by the Patent Office, and it should be noted that the actual inventor of the Class-G circuit is Mr. Tohru Sampei, of Hitachi. At one point in its development, classes of amplifiers seemed to be developing so rapidly that the company had thought to call the new circuit the "S"-system in honor of its inventor, but they settled for Class-G instead, after researching the matter thoroughly here and abroad.



"I'm afraid we'll have to take it in."

Money Generator



• **RED RASTER** pattern for checking and adjusting purity at the flip of a switch.

High level, 75 ohm video output.

- 2 year factory warranty.
- **30** day money back guarantee.

Next time repeatedly switching static and dynamic convergence patterns, think how much easier the composite HATCH-DOTS pattern be-low would make your job. It can al-so perform size, linearity, pincushion and centering checks. It's only one of sev-eral unique patterns produced by the ATC-10 that can save you time, trouble and most time, important - money. We'd love to show you how. Write us.



225 Main Street, Dept. 8C, Canon City, Colorado 81212

American Technology Corporation

Circle 36 on reader service card



This versatile mini breadboard features the same superior contacts, materials and construction we use in our full-scale ACE All Circuit Evaluators. Any solid hookup wire up to #20 plugs right in to connect DIPs, discretes and almost any components you have on hand. Super-Strip gives you 128 separate five-tie-point terminals in the circuit building matrix and 8 power and signal distribution lines — enough capacity to build circuits with as many as nine 14-pin DIPS. And when you're done with your hookup, just pull it apart — everything's as good as new. Super-Strips come with your choice of nickel-silver or gold-plated terminals. Plus an instant-mount backing and quick-removal screws for fast and easy stack-



Box 110-R Painesville, OH 44077 (216) 354-2101 Circle 13 on reader service card AUGUST 1976